A 500-Watt Multiband V.F.O. Transmitter

Figs. 6-63 through 6-71 show the circuit and other details of a 500-watt transmitter with v.f.o. frequency control, capable of operation in any band from 3.5 to 28 Mc. It is completely shielded and all tuning adjustments, including band changing, may be done with the panel controls.

As the circuit of Fig. 6-66 shows, the v.f.o. uses a 5763 in a Clapp circuit operating over a range of 3370 to 4000 kc., split into three bandspread ranges, tuned by C₁ which is fitted with a calibrated dial. These ranges, selected by proper setting of C₂, are 3500 to 3750 kc., 3370 to 3405 kc. (for 11-meter operation) and 3750 to 4000 kc, for 75-meter phone work.

The oscillator circuit is followed by two isolating stages. The first is a 6C4 connected as a cathode follower, which is very effective in reducing reaction on the oscillator by subsequent stages. Since the output of the cathode follower is quite small, it is followed by a 5763 in an amplifier fixed-tuned in the 3.5-Mc, region.

Frequency multiplying to reach the higherfrequency bands is done in the next two stages, the first using a 5763, while the second employs the larger 6146 to drive the final amplifier. These two stages are tuned with multiband tuners circuits which have a tuning range that includes all necessary bands. Thus no switching or plug-in coils are needed. Neither of these two stages is operated as a straight amplifier, except on 80 meters, Frequency is doubled in the 6146 stage for output on 40, 20 and 10 meters, and tripled for output on 15 meters. The 5763 stage is operated at 3.5 Me. for 80- and 40-meter output, doubles to 7 Me. for 20- and 15-meter output, and quadruples to 14 Me. for 10-meter output, Excitation to the final is adjusted by the potentiometer in the screen circuit of this stage.

The 813 in the final amplifier also uses a multiband tuner to cover all bands. This stage is always operated as a straight amplifier and a neutralizing circuit is provided. The only switching necessary is in the output link circuit in changing between high- and low-frequency bands. Loading is adjusted by C_{10} .

 V_8 and V_9 are used in a differential break-in keying system which automatically turns the v.f.o. on before the 5763 cathode is closed by the keyer tube V_9 , and turns the v.f.o. off after the 5763 cathode circuit has been opened. This prevents any chirp in the oscillator from appearing on the output signal of the transmitter.

A 50-ma. meter may be switched to read plate current in the exciter stages, grid current in the driver and final-amplifier stages, or screen current to the 813. The ½-ohm resistor in the 6146 high-voltage lead multiples the meter-scale reading by three, while the 1-ohm shunt in the 813 screen lead increases the full-scale reading to 100 ma. A separate 500-ma. meter is used to check plate current to the 813.

The two-circuit rotary switch, S₁, is used to bias the screens of the 6146 and 813 negative while tuning up the preceding stages and setting

Fig. 6-63 — The standard-rack panel is 12¼ inches high. Controls (National HRS) along the bottom, centers spaced at intervals of 2½ inches either side of center, are, left to right, for C₁, S₂, C₅, C₂, S₁ (Centralab 1405), S₂ and C₁₀. Power toggles are below at the center, spaced I inch apart. The calibrated v₁f.o. dial (National SCN) for C₁ is at the center, with the excitation control to the left, and the dial for C₂ to the right (both National type AM). National CFA chart frames outline the rectangular openings for the recessed meters, 50-ma, to the left, 500-ma, to the right. The shielding enclosure is built up using aluminum angle, perforated sheet (also used for the bottom plate), and sheet-metal sercess.


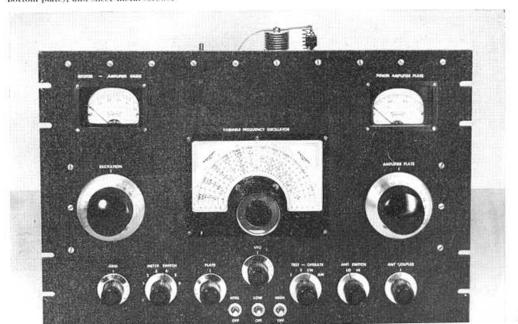


Fig. 6-64 — The components are assembled on a 17 × 12 × 3-inch aluminum chassis, The meters are housed in $4 \times 4 \times 2$ -inch boxes, the v.f.o. enclosure is $6 \times 6 \times 6$ while the box enclosing L_3 and L_4 , to the right, measures $3 \times 4 \times 5$ inches. The National R-175A r.f. choke is threaded into C_7 (Sprague 20DK-T5), C₈ (also Sprague 20DK-T5) is mounted on a metal bracket fastened to a stator terminal of Co. C12 (a Johnson N-250) connects to C₁₃ via feedthrough A. V.h.f. parasitic choke L_{10} consists of 6 turns No. 16, $\frac{1}{4}$ inch diameter, $\frac{1}{4}$ inches long. R_1 is made up of five 470-ohm 1-watt carbon resistors in parallel. It is connected across 3 turns of L_{10} . The 813 socket is mounted on ½-inch pillars over a 2¼-inch hole in the chassis. Along the rear apron are J₂, + h.v. (Millen 37001) and ground terminals, a.c. power-input connector, two a.c. outlets, low-voltage input terminals, key connector, and R_4 .

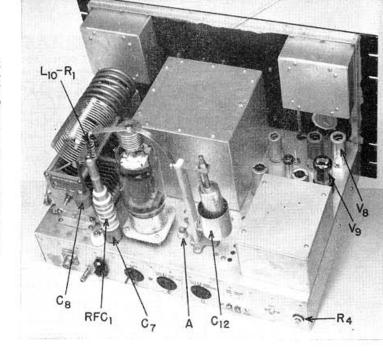

the v.f.o. to frequency. In the first position, both screens are biased; in the second position, only the 813 screen is biased, while positive voltage is applied to the screen of the 6146 so that this stage may be tuned up. In the third and fourth positions, positive voltage is applied to both screens, but in the last position it is applied to the 813 screen through an audio choke so that the stage may be screen-plate modulated.

Two bias rectifiers are included to supply fixed bias to the 6146 and 813, so that the plate currents will be cut off during keying intervals. Negative blocking voltage is also provided for the keying system. Both rectifiers operate from a single 6.3-volt filament transformer connected in reverse, The bias transformer T₂ is operated from the 6.3-volt winding of the filament transformer T₁.


Two a.c. outlets are provided for connecting the primaries of external high- and low-voltage supplies into the control circuit consisting of three toggle switches, B₁ is a ventilating blower that operates when the filament switch is closed.

It is highly important that the v.f.o. box make good contact with the chassis; otherwise the v.f.o. may be adversely affected by feedback from the adjacent final tank when working on 80 meters. Mounting screws spaced an inch around the bottom lip of the box, and correspondingly in the top cover, should eliminate this completely.

L₁ (35 μh.) is a B&W 80-BCL coil with the link and base removed. L₂ is described over Fig. 6-71. L₃ (2.6 μh.) is 31 turns of B&W 3003 Miniductor, while L₄ (5.3 μh.) is 30 turns of 3011. L₅ (1.5 μh.) consists of 11 turns of No. 16, ¾-inch diameter, 13/16 inch long. L₆ (8.9 μh.) has 29½ turns of B&W 3015 Miniductor. L₉ (1.6 μh.) has 6 turns of ¼-inch copper tubing, 2¼ inches inside diameter, 2¾ inches long.

 L_7 (4.8 μ h.) and L_8 (4.2 μ h.) are made from

Fig. 6-65 — The v.f.o. box is placed with its front wall 1346 inches back of the panel, central on the chassis, L_1 is mounted on 2-inch cones to center it in the box. The shaft of C1 (Cardwell PL-6001 minus last rotor plate) is central on the box front, at a height to match that of Co. C2 (Cardwell PL-6002) is mounted, between C₁ and the coil, shaft downward, to engage the right-angle drive below. Cs (Cardwell PL-6009) is similarly mounted, to the left of C2. Grouped to the left are V_4 , L_2 , and V_3 in front, with I's and I'1 to the rear, and I'2 in the center. Feed-throughs in the bottom of the coil box to the rear connect L₃ and L₄ to C₄ below. The ventilating holes are over the 6146. C₃ (Johnson 200DD35) is placed with its shaft 21/4 inches from the end of the chassis, and its rear end plate 1% inches in from the back edge. The three feed-throughs to the left connect Ls to S2. This photograph was made before the in-stallation of C_{12} , the R-175A choke, V_8 and In.

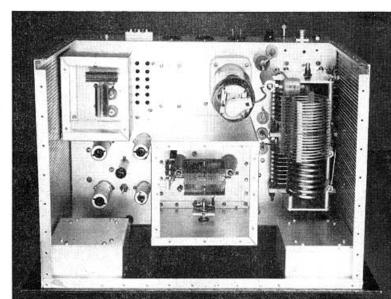

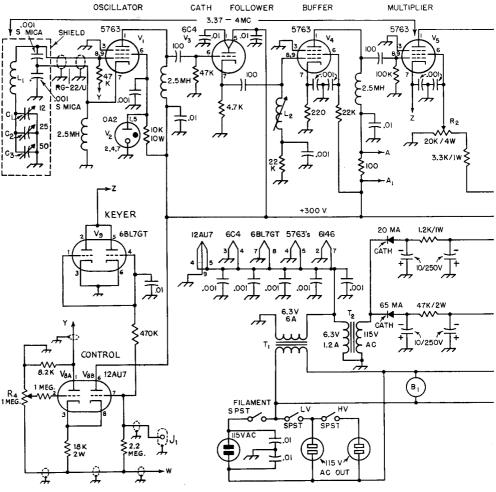


Fig. 6-66 — All capacitances less than 0.001 μ f. are in $\mu\mu$ f. All unmarked by-passes are disk ceramic. All 100-fixed capacitors are mica. All resistors are $\frac{1}{2}$ watt unless otherwise specified. RFC_2 and RFC_3 are National R C_{11} is Sprague DD60-561. Rectifiers are selenium. R_2 is the excitation control. R_3 is the oscillator-lag adjustm B_1 is the ventilating-fan motor.


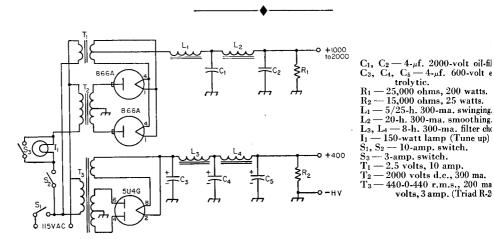


Fig. 6-67 — Circuit of a suitable power supply for the 813 transmitter.

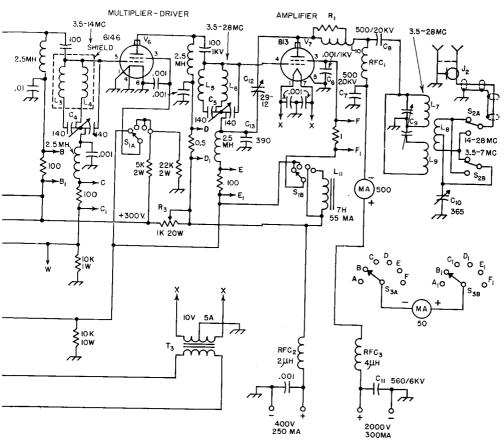

B&W 3905-1 strip coil as follows: Count off $9\frac{1}{4}$ turns, clip the wire without breaking the support bars. Bend the last quarter turn out. This portion is L_7 . Remove the next $\frac{3}{4}$ turn to make a $\frac{1}{4}$ -inch space between L_7 and L_8 . Count off 10 turns more, cut the remainder of the coil stock off. Unwind the last turn on L_8 to make the necessary lead to the stator of C_9 . Tap L_8 at the 8th turn from L_7 .

Adjustment

The diagram of a suitable power supply is shown in Fig. 6-67. The low voltage supply should deliver a full 400 volts under load, and R_3 should be adjusted eventually so that the voltage to V_1 , V_3 , V_4 and V_5 is 300 under load.

 V_{3} , V_{4} and V_{5} is 300 under load.

The v.f.o. tuning ranges should be adjusted first. Set S_{1} to the first position. Adjust R_{2} to zero and turn on the filaments and low-voltage supply. Set C_{1} at 95 degrees on the dial (near minimum capacitance). Set C_{2} accurately at midscale. Listening on a calibrated receiver, adjust C_{3} until the v.f.o. signal is heard at 3750 kc. Tune the receiver to 3500 kc., turn C_{1} toward maximum capacitance until the v.f.o. signal is heard. This should be close to the lower end of the dial. By carefully bending the rearmost stator plate of C_{1} backward, it should be possible to adjust the range of 3500 to 3750 kc. so that it covers from 5 to 95 degrees on the dial. Some slight readjustment

of C_3 may be necessary during the plate-bending process to keep the band centered on the dial.

Now set C_1 at about 15 degrees. Set the receiver at 3750 kc. and reduce the capacitance of C_2 until the v.f.o. signal is heard. Then tuning the receiver to 4000 kc., the v.f.o. signal should be heard when its dial is set at about 85 degrees. Mark this setting of C_2 accurately. If it is desired to center the 11-meter band on the dial, set C_1 at midscale. Increase the capacitance of C_2 until the v.f.o. signal is heard at 3387 kc. Mark this setting of C_2 also accurately.

When the v.f.o. frequency ranges have been set, tune the v.f.o. to 3.6 Mc. and adjust the slug of L_2 for a maximum voltage reading across the 22K grid leak of V_4 . A high-resistance voltmeter should read about -25 volts.

Readjust C_2 to midscale and turn the meter switch to read 6146 grid current, and turn up the

Tuning Chart for the 813 Transmitter								
Output Band (Mc.)	C ₄ Dial ¹ Band (Mc		Сь		C9			
3.5	8.8	3.5	6.1	3.5	77			
7	8.8	3.5	0.5	7	9			
14 21	1.5	7	9.5	14	82			
27-28	4.7	14	3.7 1.8	21 28	$\frac{26}{7}$			

 ^{1 10-}division dial — 10 max. capacitance.
 2 100-division dial — 100 max. capacitance.

excitation control to give a reading of 2 or 3 ma. Resonate the output tank circuit of the 5763 frequency multiplier at 80 meters (near maximum capacitance) as indicated by maximum 6146 grid current. Turn S₁ to the second position so that screen voltage is applied to the 6146 but not to the 813. Turn the meter switch to read 6146 plate current and resonate the 6146 output tank circuit as indicated by the plate current dip near maximum capacitance. Turning the meter switch to read 813 grid current, adjust the excitation control to give a reading of about 25 ma.

Before applying power to the 813, the neutralizing should be adjusted as described in an earlier section of this chapter. After neutralization, reduced plate voltage should be applied. Plate voltage can be reduced by inserting a 150-watt lamp in series with the high-voltagetransformer primary. A 300-watt lamp connected across the output connector can be used as a dummy load for testing. Make sure that S_2 is turned to the low-frequency position. This position is used for 3.5- and 7-Mc. operation. The other position is used for 14, 21 and 28 Me. Turn S_1 to the third position to apply screen voltage to the 813, apply plate voltage and resonate the output tank circuit (near maximum capacitance) as indicated by a dip in plate current. Full plate voltage may now be applied and C_{10} adjusted to give proper loading (220 ma. maximum). Adjust the excitation control to give an 813 grid current of 15 to 20 ma. Tuning up on the other bands is done in a similar manner, by adjusting the tuners in each circuit to the correct band to obtain the desired multiplication. The tuning chart shows the approximate dial setting for each band, but each should be checked with an absorption wave meter and the setting logged for future reference. The voltage-current chart shows typical values to be expected. The output circuit is designed for a 50- or 70-ohm resistive load. For other loads, a link-coupled antenna tuner (see transmission-line chapter) should be used.

In the keyer circuit, turning R₄ toward ground causes the oscillator to cut off more quickly after the key has been opened.

(Originally described in QST for January,

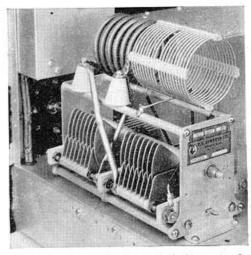


Fig. 6-68 — Close-up showing method of mounting Lτ, Ls and L₀. The stator rods of C₀ are tapped 6-32 for threaded studs by which the 1-inch cone insulators are attached. The bracket attaching C_S to the stator of C₀ is at the lower right.

1954; with modifications in the issues for June, 1954, June and October, 1956).

Tube	Band (Mc.)	Grid 1 (volts)	Grid 1 (ma.)	Grid 2 (rolts)	Grid 2 (ma.)	Cathode (volts)	Plate (volts)	Plate (ma.)
V ₁	3.5	-16		150	_	0.6	300	
Va	3.5		-	.00	-	39	300	-
V.	3.5	-18	-	190		9	300	35
V.	3.5	-64	-	115	- 5	27.5	300	5.
V.	7	-64	-	115	-	27.5	300	5
V.	14	-58		170	-	34	300	8
Ve	3.5	-75		170	-	827	400	55
Vo	7	-76		170		-	400	63
Va	14	-80		185	-	-	400	87
Vo	21	-80		195		120	400	90
V.	28	-75		175	-		400	105
V-	3.5	-165	17	400	40	-	2000	220
V.	7	-185	18	400	40	-	2000	220
V.	14	-190	19	400	35	10-01	2000	220
Vz	21	-190	20	400	35	25-31	2000	220
V.	28	-190	19	400	40	-	2000	220

* Approximately 2 ma. Depends on setting of excitation control.

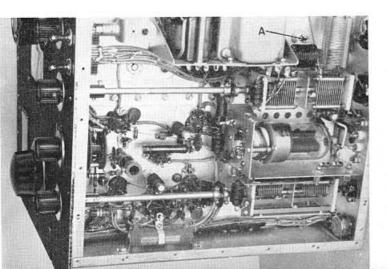


Fig. 6-69 — Detail view of the exciter section. The neutralizing lead from C₁₂ comes through the chassis at feed-through A. R₄ in the keyer circuit is in the lower right corner. R₃ is near the lower left corner. Leads to the 6146 socket pass through a large clearance hole in the bracket.

HIGH-FREQUENCY TRANSMITTERS

Fig. 6-70 — The chart frame, the panel and the aluminum box are held together, as show in A, by the hard-ware supplied with the CFA. B shows a me-ter (Triplett Model ter (Triplett Model 327-T), its insulated mounting ring, and the rear cover of the box. The meter assembly is slipped into the metal box after the latter has been attached to the rear of the panel. Shielded meter leads enter the bottom of the box through a rubber grommet. The shield braid should be bonded to the outside of the aluminum case at the point of entry.

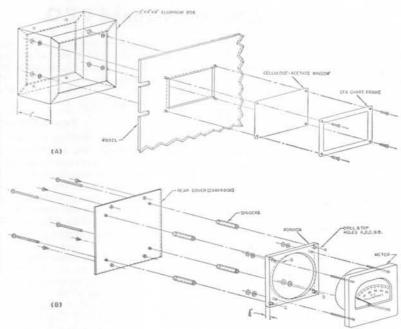


Fig. 6-71 — The panel drops $\frac{3}{16}$ inch below the bottom edge of the chassis. The National RAD right-angle drive for C_2 is at the center. The other controls along the bottom are placed $1\frac{1}{2}$ inches up from the bottom edge of the chassis, and the corresponding components mounted so that their shafts line up with the controls. Panel bushings should be provided for the shafts of C_{10} (Cardwell PL-7006), and the right-angle drive; panel-bearing shaft units for C_4 and C_5 (Cardwell PL-6043), and S_2 (Centralab RR wafer on P-121 index assembly). The 6146 is mounted on a $5 \times 2\frac{1}{4}$ -inch bracket between C_4 and C_5 , whose shafts are fitted with insulating couplings, C_5 is mounted on spacers, while C_4 is mounted on its side on a bracket. T_1 (Triad F-18A) and T_2 (Triad F-14X) are mounted on another bracket at the center. L_5 and L_6 , at right angles, are soldered between the terminals of C_5 and Pin 4 of the 813 socket, seen through the $2\frac{1}{4}$ -inch hole in the chassis. C_{10} and S_2 are mounted on small brackets. T_3 (Triad F-23U) and the blower (available from Allied Radio, Chicago, No. 72P715) are to the left. The screwdriver-slotted shaft of C_5 and be seen between the shaft of C_5 and the shielded power wires to the left. All power wiring is done with shielded wire (Belden 8656, Birnbach 1820, or shielded ignition wire for the 2000-volt line; Belden 8885 for the rest). L_2 , behind S_3 (Centralab 1411), is a National XR-50 slug-tuned form close-wound with 93 turns No. 36 enameled wire.

